

### Problems:

Question (11)

- 1.) Find the gain of a non-inverting amplifier if  $R_f = 10k\Omega$  and  $R_1 = 1k\Omega$

Given:  $R_f = 10k\Omega$

$R_1 = 1k\Omega$

W.k.t the output of a non-inverting amplifier is

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_{in}$$

Here Gain is  $A = 1 + \frac{R_f}{R_1}$   $\left[ \frac{V_o}{V_{in}} = A \right]$

$$A = 1 + \frac{10}{1}$$

$$\boxed{A = 11}$$

- 2.) A non-inverting amplifier has closed loop gain of 25. If input voltage  $V_i = 10mV$ ,  $R_f = 10k\Omega$  determine the value of  $R_1$  and output voltage  $V_o$

Given: The closed loop gain  $A = 25$

$V_i = 10mV$ ,  $R_f = 10k\Omega$

W.k.t, for a non-inverting amplifier.

$$\text{Gain } A = 1 + \frac{R_f}{R_1}$$

Given  $A = 25$

P.T.O

Problem 2 continued . . . .

Hence

$$1 + \frac{R_f}{R_1} = 25$$

$$\frac{R_f}{R_1} = 25 - 1 = 24$$

Hence.

$$R_1 = \frac{R_f}{24} = \frac{10 \text{ k}\Omega}{24} = 416.67 \Omega$$

The output voltage  $V_o$

$$V_o = V_{in} \left( 1 + \frac{R_f}{R_1} \right)$$

$$= 10 \text{ mV} \times 25$$

$$V_o = 250 \text{ mV}$$

3.) Design an inverting and non-inverting operational amplifier to have a gain of 15.

Given:  $A = 15$

For an inverting amplifier  $V_o = \frac{-R_f}{R_1} V_{in}$


$$\text{Gain } \frac{R_f}{R_1} = 15$$

$$R_f = 15 R_1$$

$$\text{Take } \boxed{R_1 = 1 \text{ k}\Omega}$$

$$\text{then } \boxed{R_f = 15 \text{ k}\Omega}$$

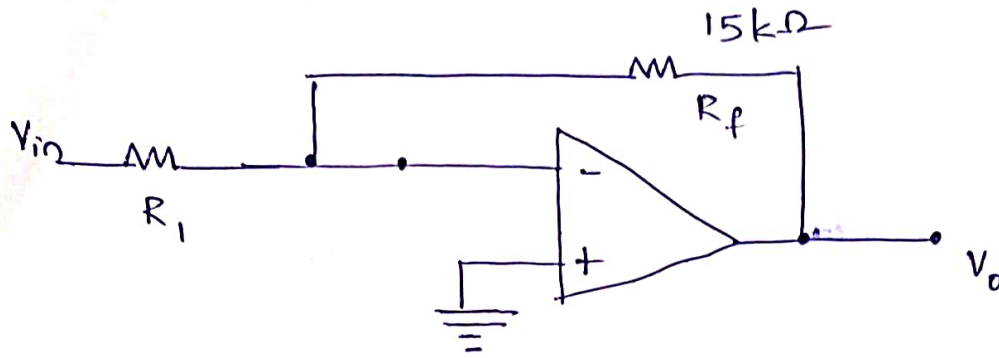The designed circuit can be drawn as below.



For non-inverting amplifier,

$$V_o = \left( 1 + \frac{R_f}{R_1} \right) V_{in}.$$

Given gain = 15

$$1 + \frac{R_f}{R_1} = 15$$

$$\frac{R_f}{R_1} = 15 - 1 = 14$$

$$R_f = 14 R_1$$

Take  $R_1 = 1k\Omega$

Then  $R_f = 14k\Omega$

Designed circuit

